 


Sequential Logic



Building a Modern Computer From First Principles


www.nand2tetris.org

Sequential VS combinational logic


- **Combinational devices:** operate on data only; provide calculation services (e.g. Nand ... ALU)
- **Sequential devices:** operate on data and a clock signal; as such, can be made to be *state-aware* and provide storage and synchronization services
- Sequential devices are sometimes called "clocked devices"
- The low-level behavior of clocked / sequential gates is tricky
- The good news:
 - All sequential chips can be based on one low-level sequential gate, called "data flip flop", or DFF
 - The clock-dependency details can be encapsulated at the low-level DFF level
 - Higher-level sequential chips can be built on top of DFF gates using combinational logic only.

Lecture plan

 
- Clock
- A hierarchy of memory chips:
 - Flip-flop gates
 - Binary cells
 - Registers
 - RAM
- Counters
- Perspective.



 - In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)
- In real hardware, the clock is implemented by an oscillator
- In our hardware simulator, clock cycles can be simulated either
 - Manually, by the user, or
 - "Automatically," by a test script.



 
- A fundamental state-keeping device
- For now, let us not worry about the DFF *implementation*
- Memory devices are made from numerous flip-flops, all regulated by the same master clock signal
- Notational convention:




1-bit register (we call it “Bit”)

Objective: build a storage unit that can:

 - (a) Change its state to a given input
- (b) Maintain its state over time (until changed)




 if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)



out(t) = in(t-1)


Basic building block

 

out(t) = out(t-1) ?
out(t) = in(t-1) ?


Won't work

Interface

 


if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

Implementation

 


- Load bit
- Read logic
- Write logic

Multi-bit register

 

if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

1-bit register

 

if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

w-bit register


- Register's width: a trivial parameter
- Read logic
- Write logic

Relevant topics from the HW simulator tutorial:

- Clocked chips: When a clocked chip is loaded into the simulator, the clock icon is enabled, allowing clock control
- Built-in chips:
 - feature a standard HDL interface yet a Java implementation
 - Provide behavioral simulation services
 - May feature GUI effects (at the simulator level only).


Random Access Memory (RAM)

HW
simulator
demo

 

- Read logic
- Write logic.

RAM interface

 


```
Chip name: RAMn // n and k are listed below
Inputs:   in[16], address[k], load
Outputs:  out[16]
Function:  out(t) = RAM[address(t)](t)
           If load(t-1) then
               RAM[address(t-1)](t) = in(t-1)
Comment:  "=" is a 16-bit operation.
```

The specific RAM chips needed for the Hack platform are:

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14


RAM anatomy

 

Counter

Needed: a storage device that can:

 - (a) set its state to some base value
- (b) increment the state in every clock cycle
- (c) maintain its state (stop incrementing) over clock cycles
- (d) reset its state




```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

- Typical function: *program counter*
- Implementation: register chip + some combinational logic.


Recap: Sequential VS combinational logic

Combinational chip

 


$out = \text{some function of } (in)$

Sequential chip

 


$out(t) = \text{some function of } (in(t-1), out(t-1))$

Time matters

 

 - During a tick-tock cycle, the **internal states** of all the clocked chips are allowed to change, but their **outputs** are “latched”
- At the beginning of the next cycle, the **outputs** of all the clocked chips in the architecture **commit** to the new values.



Implications:

- ❑ Challenge: propagation delays
- ❑ Solution: clock synchronization
- ❑ Cycle length and processing speed.


Perspective

- All the memory units described in this lecture are standard
- Typical memory hierarchy

- SRAM ("static"), typically used for the cache
- DRAM ("dynamic"), typically used for main memory
- Disk

(Elaborate caching / paging algorithms)

 - A Flip-flop can be built from Nand gates
- But ... real memory units are highly optimized, using a great variety of storage technologies.



End notes: some poetry about the limits of logic ...

*There exists a field where things are neither true nor false;
I'll meet you there. (Rumi)*

*In the place where we are always right
No flowers will bloom in springtime (Yehuda Amichai)*

*A mind all logic is like a knife all blade;
It makes the hand bleed that uses it.
(Rabindranath Tagor)*